

ECE-4710 / 5710 · COMPUTER HARDWARE DESIGN · WINTER 2026

RGB LED Color Control

Using PWM with an Accelerometer, Temperature Sensor, and Switch Inputs

Yousif Fatohi

Andrew Kashat

Sedim Baffrow

Peter Younan

INSTRUCTOR

Prof. Daniel Llamocca

PRESENTATION

April 23, 2026

TARGET

Digilent Nexys-4 DDR · Artix-7 XC7A100T

What the Circuit Does

Tilt the board, warm the chip — watch the LED change color.

Three sensor outputs are read from the onboard ADXL362 via SPI, and are mapped to the RGB LED's three color channels. The ADXL362's X-axis output drives the red channel, the Y-axis drives the green channel, and the IC's temperature drives the blue channel. Nine slide switches allow the user to set a minimum brightness floor for each color channel: off, about 25%, about 50%, or about 75%.

CONTROL

3-state FSM (S1 → S2 → S3)

DATAPATH

3 × 16-bit regs + Map To Max blocks
+ 3 × PWM



RED

X-axis tilt

LD16_R



GREEN

Y-axis tilt

LD16_G




BLUE

Chip temperature

LD16_B

System Block Diagram

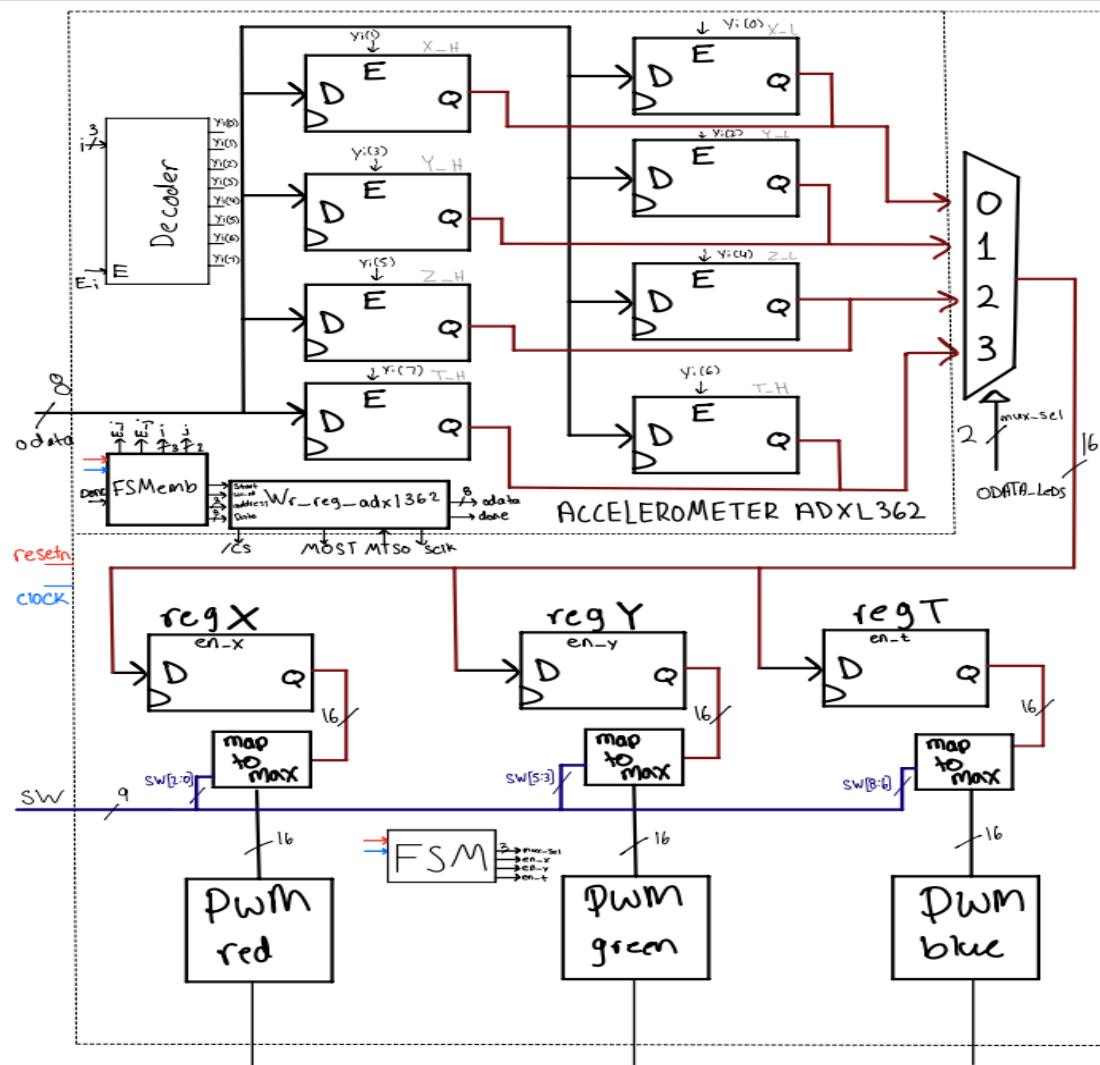

One Full Cycle Through the Pipeline



Three latch states, three axes

S1 latches X (Red), S2 latches Y (Green), S3 latches Temp (Blue). On each valid read, the FSM cycles through X, Y, and Temp.


Registers smooth the output

In between sample sets, each register retains its value, meaning that there is no flickering due to waiting for new PWM values.

Switches shape the response

For each channel, three switches decide priority encoding of a minimum brightness setting of either off, 25%, 50%, or 75%. However, the real-time sensor signal (with scaling of ×64 and saturation) can brighten using max().

FSM — Our 3-State FSM

 

FUNCTION

Cycles through X, Y, and Temp one axis per clock, steering the accelerom mux and pulsing the right register enable so each sample lands in its own latch.

State outputs

S1 sel = "00" en_x = 1 latch X → Red

S2 sel = "01" en_y = 1 latch Y → Green


S3 sel = "11" en_t = 1 latch T → Blue

What's happening: This is the only FSM designed by our group. It is quite minimal in design: no calculation or any decision making; only sequencing is involved. On every valid pulse on FSMemb, our 3-state FSM goes through transitions of S1 to S2 to S3 and back to S1. In doing so, we enable sel [1:0] and the one-hot registers for each axis.

Holding Registers — regX / regY / regT

FUNCTION

 Three 16-bit clock-enable registers capture each axis's latest sample and hold it steady, so the PWM downstream always has a valid duty.



regX

CLOCK ENABLE

en_x

16-bit

→ Red PWM

regY

CLOCK ENABLE

en_y

16-bit

→ Green PWM

regT

CLOCK ENABLE

en_t

16-bit

→ Blue PWM


Reset behavior: synchronous, active-low · on resetn = '0', all three registers clear to 0x0000 — LED starts dark.

What's happening: The three registers separate the slower sampling process from the faster clock rate for PWM. The PWM module requires a new duty cycle on every system clock pulse, while new samples occur only after several microseconds; the registers compensate for this time discrepancy by keeping the latest data sampled until a new sample occurs.

Map To Max — Switch Floors

+ Sensor, Combined

Three combinational stages per channel

 

Switch allocation (9 switches · 3 per channel)

SW[2:0] → RED floor

SW[5:3] → GREEN floor

SW[8:6] → BLUE floor

1 Absolute value – BASELINE

Pick $|value|$ sufficiently negative for negative tilt to have the same brightness as positive tilt. Now subtract $BASELINE = 150$ (saturated to zero) to eliminate the DC offset from the temperature sensor value. Red and green operate with $BASELINE = 0$.

2 Shift left 6 (×64) with saturation

Left-shift by 6 (multiply by 64) to convert the value into an 8-bit format. If the operation would cause a 16-bit overflow (top bit set) the result will be saturated to $0xFFFF$. It is precisely this which gives us 'full tilt = full brightness'.

3 max(switch floor, scaled sensor)

Switches pick a brightness FLOOR (see table). Whichever is larger — the floor or the live sensor — wins. If $sw = 000$, output is forced to 0 regardless.

Brightness floor per switch code

SWITCH	DUTY (hex)	LOOKS LIKE
"000"	0x0000	OFF
"001"	0x1000	~25% bright
"010"/"011"	0x4000	~50% bright
"1xx"	0x9000	~75% bright

What's happening: Switches select a minimum brightness value. The live sensor is multiplied by 64 and saturated to $0xFFFF$, and whichever is larger determines the final result. That means that the user can force any one channel to be lit with one of four brightnesses (off / 25% / 50% / 75%), but no more than the sensor will let him/her. $sw=000$ forces hard-off.

PWM — 3-Channel Pulse-Width Modulator

How one instance works


A 16-bit counter runs from 0 up to $TPWM - 1$, then rolls over.

A comparator checks $counter < duty$. When it is true, the output is '1' — otherwise '0'.

$duty = 0 \rightarrow LED \text{ off}$ $duty = TPWM \rightarrow LED \text{ full on.}$

Project settings

TPWM	65535 (fixed)
Counter width	16 bits
Duty input	from Map To Max
PWM freq.	~1.53 kHz
Why 1.5 kHz	well above flicker

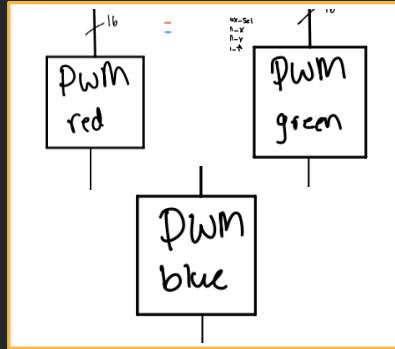

Three instances drive LD16_R / G / B

PWM RED

LD16_R

$duty \leftarrow \max(\text{floorR}, |x_reg| \times 64)$



PWM GREEN

LD16_G

$duty \leftarrow \max(\text{floorG}, |y_reg| \times 64)$



PWM BLUE

LD16_B

$duty \leftarrow \max(\text{floorB}, |(t_reg - 150)| \times 64)$



What's happening: In the PWM module section, the duty cycle number that is purely digital becomes light. The human eye will average out the on-off cycle at around 1.5 kHz; therefore, 25% duty will appear as quarter bright, while 75% duty will appear as three-quarters bright. There are three modules using the same clock and TPWM.

Testbench & Hardware Setup

Testbench — `tb_top_rgb_ctrl`

● Clock / reset

Clock at 100 MHz (10ns period). Keeps `resetsn` low for 100 ns to initialize all the registers and set FSM in S1, then frees it.

● Switch stimulus

Runs through 10 SW states - 25%, 50%, 75% floors for each color, off, all channels 25%, all channels 75%, and some combinations. Each state is kept active for 800 μ s, so there's always one complete 655 μ s PWM cycle on display.

● MISO pattern driver

We send a 32-bit repeating pattern (0x1A2B3C4D) through MISO, one bit per clock pulse. So each byte read from SPI by FSMemb will be unique and non-zero. This helps us track signals along `regX/Y/T` throughout the whole process.

● What we verify in the waveform

No assertions here, just visual inspection. We check FSM state transitions (S1 \rightarrow S2 \rightarrow S3), one-hot enables, register latch, and that each LED duty is correct for their switch floor for all possible SW states.

Hardware setup

Board	Digilent Nexys-4 DDR
FPGA	Artix-7 XC7A100T
Sensor	On-board ADXL362 accelerometer + die temp
Output	RGB LED LD16 (R, G, B pins)
Clock	100 MHz on-board oscillator
Switches	SW[8:0] — 9 slide switches
Toolchain	Vivado · Vivado Simulator
Language	VHDL · IEEE.NUMERIC_STD

What's happening: Prior to loading anything on the board, we simulate our design using `tb_top_rgb_ctrl`. Testbench sets up `resetsn`, SW switches, and generates a cyclic pattern on MISO (with `SCLK_T = 16` so SPI operates faster in sim). Then we inspect all internal signals - FSM state, enables, registers, duties.

Waveform — Three FSM Cycles in Sim



State order holds

state cycles S1 → S2 → S3 → S1 ... one state per clock, forever.

Enables fire one-hot

en_x in S1, en_y in S2, en_t in S3. Never two high at once.

Registers latch on time

regx / regy / regT update only when their enable pulses.

What's happening: Three complete FSM cycles have been captured in this wave form in the Vivado simulation tool. First observe the state, then the three enables, followed by the three registers; notice that each axis gets loaded into its respective register only when its corresponding enable pulse occurs.

Results & What We Learned

MAIN STRUGGLE

Calibrating the blue baseline

At room temperature, the ADXL362's onboard temperature sensor output does not read zero; its DC output is a large positive number that changes only very little with an increase in temperature. Without correction, the LED would blink with full intensity at higher temperatures, indicating a change in temperature, which was not the goal here.

OUR FIX: Subtract a BASELINE of 150 from the Map To Max block before the shift operation. Room temperature silicon is interpreted as zero intensity; the LED brightness increases as the silicon heats.

WHAT WE LEARNED

About our own design decisions

Baseline subtraction beats scaling alone

Offset shifting the DC signal only increases the offset. Removal of the offset is what makes the channel sensitive to levels and not offsets.

Using a BASELINE generic kept one component

Rather than develop another function to scale with temperature, Map To Max was parameterized; the same algorithm, three different versions, where blue was set to BASELINE = 150.

Fixed $\times 64 + \max()$ is cheap and stable

The sensor gain was fixed to $\times 64$, and the priority encoder switch floor were fixed, combined by $\max()$ function – no shifting required, no varying TPWM value. The PWM period remained constant for all switch positions, eliminating any LED flickering during user adjustment.

Saturation is on purpose

Capping the value at 0xFFFF in case of an overflow allows the user to have predictable behavior at maximum brightness instead of wraparound behavior to a random low color.

Live Demo

What you'll see in the video

- 1 Flat board, switches mid-range → steady baseline color.
- 2 Tilt along X → red intensity tracks the tilt angle.
- 3 Tilt along Y → green intensity tracks independently.
- 4 Warm the chip by touch → blue channel slowly climbs.
- 5 All switches up → saturated, maximum brightness.

